

**IMPORTANT TERMS:**

- Circuit
- In parallel
- In series
- Parallel circuit
- Schematic diagram
- Series circuit

**EQUATIONS:**

$$\text{current} = \frac{\text{voltage}}{\text{resistance}}$$

$$I = \frac{V}{R}$$

$$1 \text{ ampere} = 1 \frac{\text{volt}}{\text{ohm}}$$

**Series Circuits**

$$I = \frac{V_{\text{source}}}{R}$$

$$V_{\text{tot}} = V_A + V_B + \dots$$

$$R = R_A + R_B + \dots$$

**Parallel Circuits**

$$I_A = \frac{V}{R_A}$$

$$V_{\text{tot}} = V_A = V_B = V_C = \dots$$

$$I = I_A + I_B + I_C$$

$$\frac{1}{R} = \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}$$

# UNIT V: Electricity and Magnetism

## Chapters 32-37

### Chapter 35: Electric Circuits

#### I. A Battery and a Bulb (35.1)



A. **Circuit**- A complete \_\_\_\_\_ for electrons to \_\_\_\_\_

1. Flow of \_\_\_\_\_ like flow of **water** in a closed system of pipes

a. The **battery** would be analogous to the \_\_\_\_\_

b. **Wires** analogous to the \_\_\_\_\_

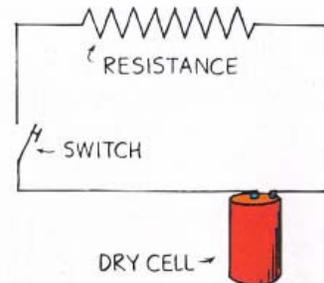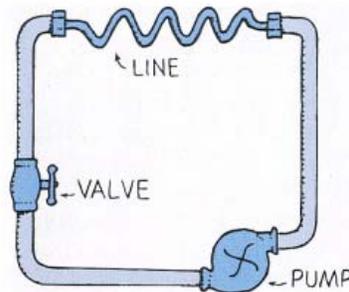B. The water flows through the pump and the \_\_\_\_\_ flow through the battery



#### II. Electric Circuits (35.2)

A. **Electric Circuit**- any path along which \_\_\_\_\_ can flow

1. Must be a complete circuit with **no** \_\_\_\_\_

2. Gap usually provided by **electric** \_\_\_\_\_

B. Most circuits have more than one device that receives electrical energy. Devices can be connected in a circuit in one of two ways, \_\_\_\_\_ or \_\_\_\_\_.

#### III. Series Circuits(35.3)

A. Electric current has but a \_\_\_\_\_ **pathway** through a series circuit. **Current is the** \_\_\_\_\_ through each electrical device in the circuit



B. The **total resistance** to current in the circuit is the \_\_\_\_\_ **of the individual resistances** along the circuit path

C. The current in the circuit is equal to the **voltage supplied** by the source divided by the **total** \_\_\_\_\_ of the circuit (in accord with Ohm's law)





D. The **total voltage** impressed across a series circuit \_\_\_\_\_ among the electrical devices in the circuit so that the sum of the "voltage drops" across each device is equal to the total voltage supplied by the source.

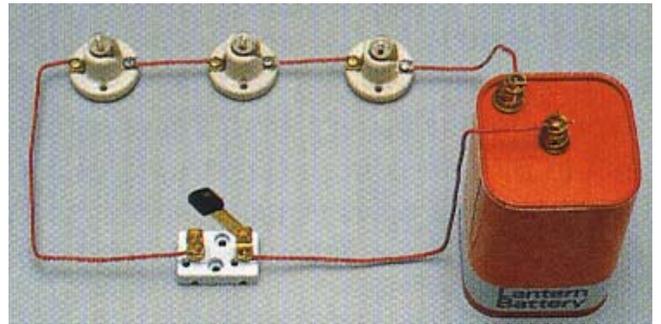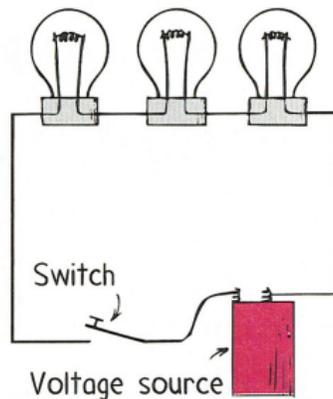E. The **voltage drop across each device is proportional to its** \_\_\_\_\_. This follows from the fact that more energy is wasted as heat when a current passes through a high-resistance device than when the same current passes through a device offering little resistance.




#### IV. Parallel Circuit (35.4)

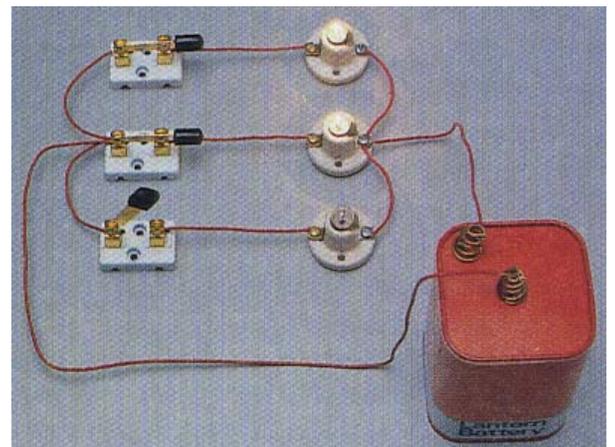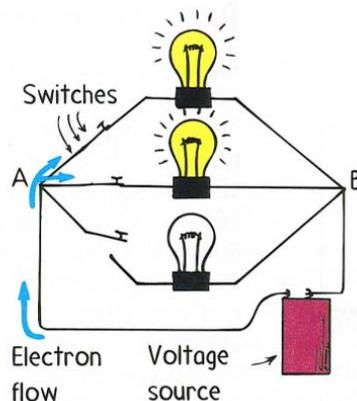A. Each device connects the **same two points A and B** of the circuit. The **voltage is therefore the** \_\_\_\_\_ **across each device**




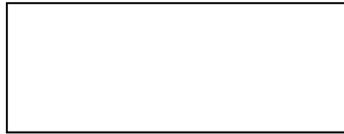B. The **total current** in the circuit \_\_\_\_\_ among the **parallel branches**. Because the **voltage across each branch is the same**, the **amount of current in each branch is inversely proportional to the resistance of the branch**



Remember that the voltage is the same across each of the branches

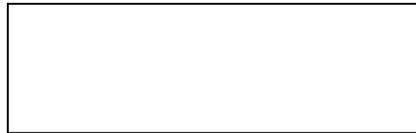C. The **total current in the circuit equals the \_\_\_\_\_ of the currents in its \_\_\_\_\_ branches**



Where  $I_A, I_B, I_C$  are currents through the branches and  $I$  is the total current


D. **As the number of parallel branches is increased, the overall resistance of the circuit is \_\_\_\_\_** (just as more check-out cashiers at a supermarket decreases people-flow resistance). With each added parallel path, the overall circuit resistance is lowered. This means the **overall resistance of the circuit is \_\_\_\_\_ than the resistance of any one of the \_\_\_\_\_.**





## V. Schematic Diagrams (35.5)

A. **Schematic diagram**- simple diagrams to represent electrical circuits.

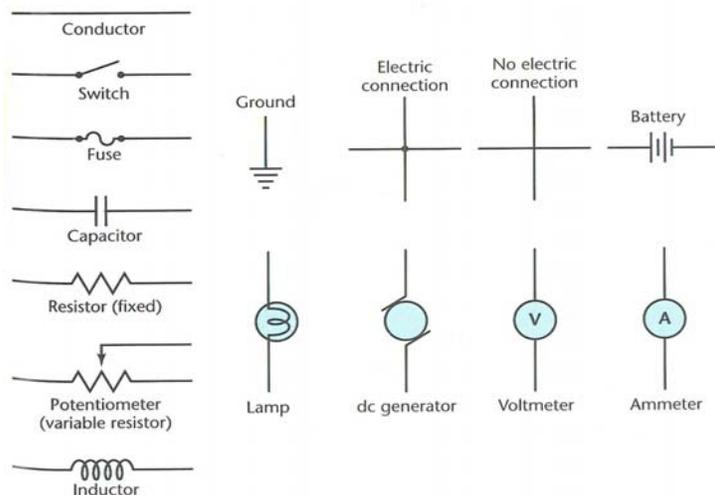1. **Symbols** used to represent certain circuit elements
2. **Circuit diagrams (schematics) show electrical connections, not the \_\_\_\_\_ layout**
3. Common Symbols:



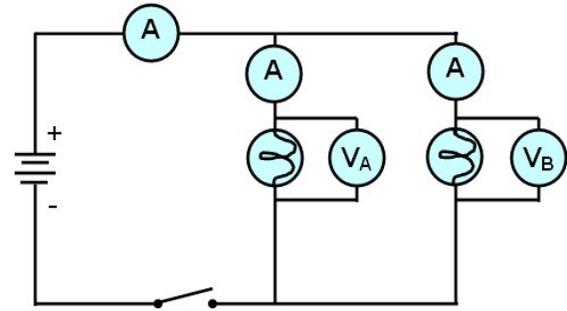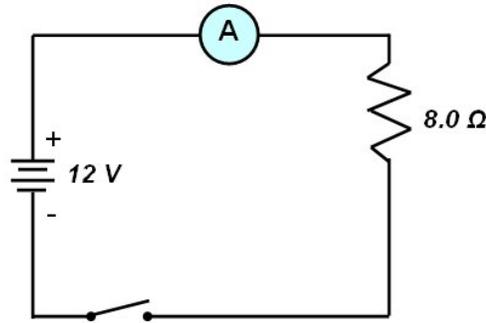B. Examples of **Series** and **Parallel** circuits



VI. Combining Resistors in a Compound Circuit (35.6)


A. Sometimes it is useful to know the \_\_\_\_\_ **resistance** of a circuit that has several resistors in its network

1. **Equivalent resistance**- value of the single resistor that would comprise the same \_\_\_\_\_ to the battery or power source

2. Calculate using the rules for \_\_\_\_\_ resistors in series and parallel

B. Series circuits-


$$R = R_A + R_B$$

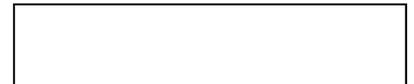

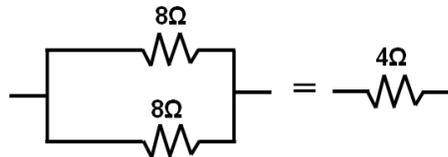C. Parallel circuits-

$$\frac{1}{R} = \frac{1}{R_A} + \frac{1}{R_B} + \dots$$

$$\frac{1}{R} = \frac{1}{8} + \frac{1}{8} = \frac{2}{8}$$



VII. Parallel Cir-  
loading (35.7)

uits and Over-

A. When add more devices (pathways) in house, the combined **resistance** is \_\_\_\_\_ in the circuit

1. Therefore, greater amount of \_\_\_\_\_ occurs
2. Can overload circuit and may result in \_\_\_\_\_ (fire)

B. Connect fuses in series along supply line to protect (fuse or circuit breaker prevents \_\_\_\_\_)